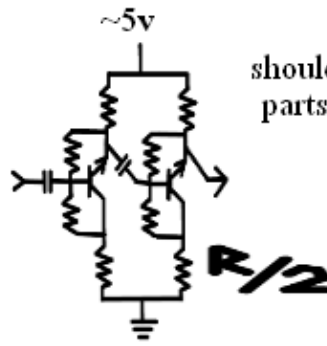
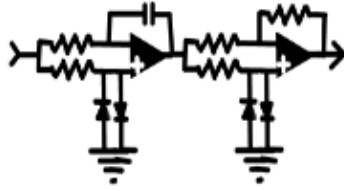


2 kinds of waveshaper/nonlinearities  
both doing frequency tripling



all R's equal, except where noted.  
should be very tolerant of different kinds of  
parts and supply voltages.

the opamp supply voltages  
can act as control voltages over  
the waveshaping function

to be preceded by some version of this fuzz frequency 1/3 divider

